

Management and analysis of physics datasets, Part. 1

Third Laboratory

Antonio Bergnoli bergnoli@pd.infn.it

25/11/2019



Laboratory Introduction



- make some practice with sequential circuits.
- Exploit the configuration flash memory chip of the Arty7 board.



VHDL naming convention


Signals/components	Name
Clock	<i>clk</i>
Reset	<i>rst</i>
Input Port	<i>port_in</i>
Output Port	<i>port_out</i>
VHDL file name	<i>entityname.vhd</i>
Test bench file name	<i>tb_entityname.vhd</i>
Signal between 2 comps	<i>sign_cmp1_cmp2</i>
process name	<i>p_name</i>
...	...



Sequential Logic Circuits



Glitch (1)

 


$$Y = A \text{ and } (\text{not } A) = '0'$$

So far we have assumed that the logic gates do not introduce a delay. In practice this does not happen.



Glitch (2)

 

Actually there is a brief delay between the input changing and the respective changing.
The spurious '1' is a **glitch**.



How reduce glitches ?

- With extra combinatorial hardware. This design is not so simple.
- Design circuit glitches free. The logic: wait a certain amount of time, during with you do not consider the glitches. This is the idea behind the clocked circuits or **sequential circuits**.

Are they a problem? Depends on the circuit downstream the glitch. I.e., if there is a pulse counter, the final result of the counter will be wrong.



Sequential Elements - Code

```
entity cmb_clk is
  Port (clk : in std_logic;
        rst : in std_logic;
        a_in : in std_logic;
        ab_in : in std_logic;
        cmb_out : out std_logic;
        ltch_out : out std_logic;
        ff_out : out std_logic);
end cmb_clk;
```

```
architecture rtl of cmb_clk is
```

```
begin
```

```
p_ff: process(clk, rst, a_in, ab_in) is
```

```
begin
```

```
if rst = '1' then
```

```
ff_out <= '0';
```

```
elsif rising_edge(clk) then
```

```
ff_out <= a_in and ab_in;
```

```
end if;
```

```
end process;
```

```
p_ltch: process(clk, rst, a_in, ab_in) is
```

```
begin
```

```
if rst = '1' then
```

```
ltch_out <= '0';
```

```
elsif clk = '1' then
```

```
ltch_out <= a_in and ab_in;
```

```
end if;
```

```
end process;
```

```
cmb_out <= a_in and ab_in;
```


FLIP-FLOP

LATCH

COMBINATORIAL



Sequential Elements - Schematic

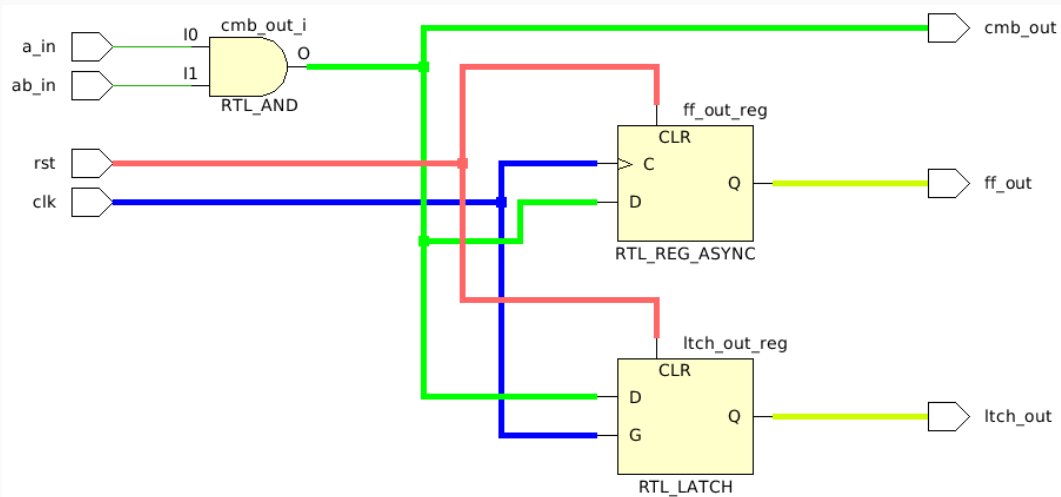

Sequential Elements - Testbench

```
architecture Behavioral of tb_cmb_clk is
  component cmb_clk is
    Port (clk : in std_logic;
          rst : in std_logic;
          a_in : in std_logic;
          ab_in : in std_logic;
          cmb_out : out std_logic;
          ltch_out : out std_logic;
          ff_out : out std_logic);
  end component;

  signal clk,rst : std_logic; signal a,ab : std_logic; signal cmb,ltch,ff : std_logic;

begin

  uut : cmb_clk port map (clk=> clk, rst => rst, a_in => a, ab_in => ab, cmb_out => cmb, ltch_out => ltch, ff_out => ff);

  p_clk : process -- 100 MHz
  begin
    clk <= '0'; wait for 5 ns; clk <= '1'; wait for 5 ns;
  end process;

  p_rst : process
  begin
    rst <= '1'; wait for 15 ns; rst <= '0'; wait;
  end process;


  p_cmb : process
  begin
    a <= '0'; wait for 0.2 ns; ab <= '1'; wait for 67 ns;
    a <= '1'; wait for 0.2 ns; ab <= '0'; wait for 67 ns;
  end process;

end Behavioral;
```

NOT delay



Sequential Elements - Simulation

 

- A latch is sensitive to the level. In this example to '1'.
- A Flip-Flop is sensitive to the edge. In this example to the rising edge $0 \rightarrow 1$.
- A Flip-Flop is immune to glitches.
- In the next laboratories you use the Flip-Flops !!!



- Inside a process the code lines are executed sequentially. Inside a process the code, you consider the behavior similar to C, Python ...
- The processes run in parallel.
- In the sensitivity list of a process, you write all their inputs .
- In the testbench file is good practice to use a process for the clock signal, one for the reset signal and one for the others signals.



Notes on the Clock and Reset

- In this laboratory you use an asynchronous reset.

```
if rst = '1' then
    .
    .
    .
elseif rising edge(clk) then
    .
    .
    .
end if;
```

- It is used to bring the circuit in a known state. That is the states (you will learn) and the output of the circuit are set to a default value.
- The clock in the board is provided by an oscillator at 100 MHz. It is connect to the pin E3 of the FPGA.

```
set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { clk }]; #IO_L12P_T1_MRCC_35 Sch=gclk[100]
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports { clk }];
```



Counter



Counter and Led Blink

```
use IEEE.NUMERIC_STD.ALL;

entity blink is
  Port (clk : in std_logic;
        rst : in std_logic;
        y_out: out std_logic);
end blink;

architecture rtl of blink is
  signal counter : unsigned (27 downto 0);
begin
  p_cnt: process(clk, rst) is
    begin
      if rst = '1' then
        counter <= (others => '0');

      elsif rising_edge(clk) then
        counter <= counter + 1;
      end if;
    end process;

    y_out <= counter(26);
  end rtl;
```

$$f_{\text{blink}} = \frac{f_{\text{clock}}}{2^{26}} = \frac{100\text{MHz}}{2^{26}}$$

Slower Counter

```
use IEEE.NUMERIC_STD.ALL;
entity cnt is
  Port (clk : in std_logic;
        rst : in std_logic;
        y_out: out std_logic_vector(3 downto 0));
end cnt;
architecture rtl of cnt is
  signal slow_clk, slow_clk_p : std_logic; signal counter : unsigned (27 downto 0);
  signal slow_counter : unsigned (3 downto 0);
begin
  p_cnt: process(clk, rst) is
  begin
    if rst = '1' then
      counter <= (others => '0');
    elsif rising_edge(clk) then
      counter <= counter + 1;
    end if;
  end process;
  slow_clk <= counter(26);
  p_slw_cnt: process(clk, rst, slow_clk) is
  begin
    if rst = '1' then
      slow_counter <= (others => '0');
    elsif rising_edge(clk) then
      slow_clk_p <= slow_clk;
      if slow_clk = '1' and slow_clk_p = '0' then -- "RISING EDGE"
        slow_counter <= slow_counter + 1;
      end if;
    end if;
  end process;
  y_out <= std_logic_vector(slow_counter);
end rtl;
```

Slower Counter - few changes

1. Use *btn0* as the reset button;
2. Use *sw0* to change the counter incremental. If *sw0* = '0' the counter increment itself, else it decrements itself.
3. Use *sw1* to freeze the led status. If *sw1* = '1' the counter is stuck.

In order to simulate with a testbench the entity *cnt*, *slow_clk* signal would be assigned at *counter*(3).

Then you create the bitstream and you download it into the FPGA.



Use of the SPI Flash Memory




- You noticed that when the board is programmed and you power off it, at the boot afterward the board has been reset.
- To avoid this, you have to load the configuration file (.mcs) in the SPI flash memory.
- So at the next boot, the FPGA loads the configuration file from the flash, without waiting you load the bitstream.

In the next slides is described how to generate the mcs file and how to load it in the flash memory.




Flash Chip

 

Flash configuration (1) Tools → Generate Memory


Configuration File →

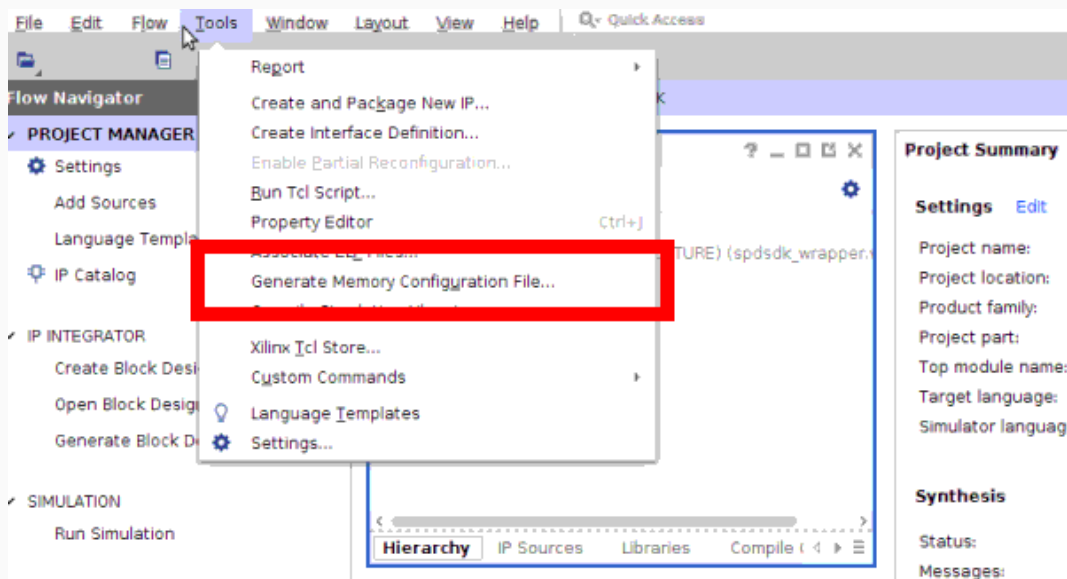

[ide]


Flash configuration (2) Check "Memory Part", click "...", search

"mt25ql128-spi-x1_x2_x4" and "OK".

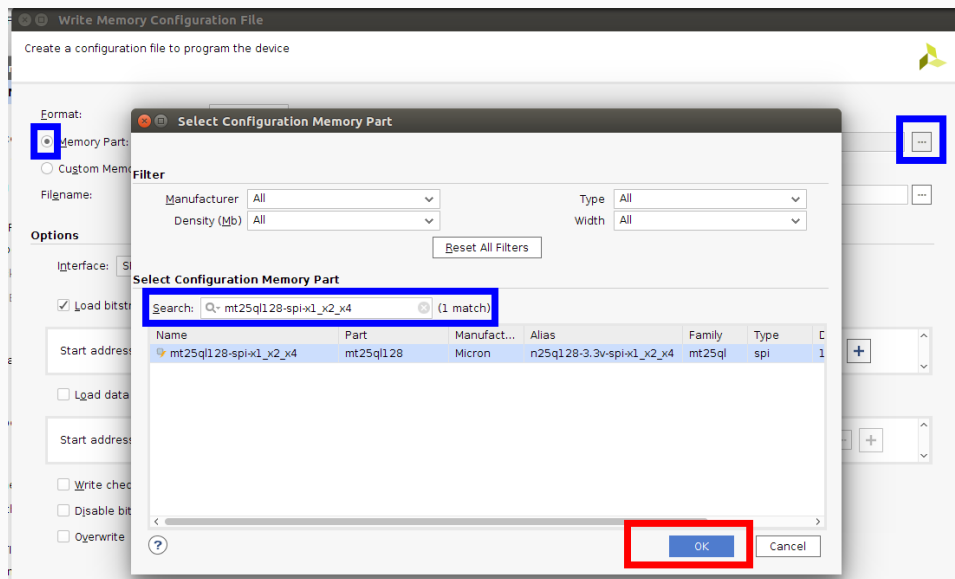

Flash configuration (2) Check "Memory Part", click "...", search

"mt25ql128-spi-x1_x2_x4" and "OK".

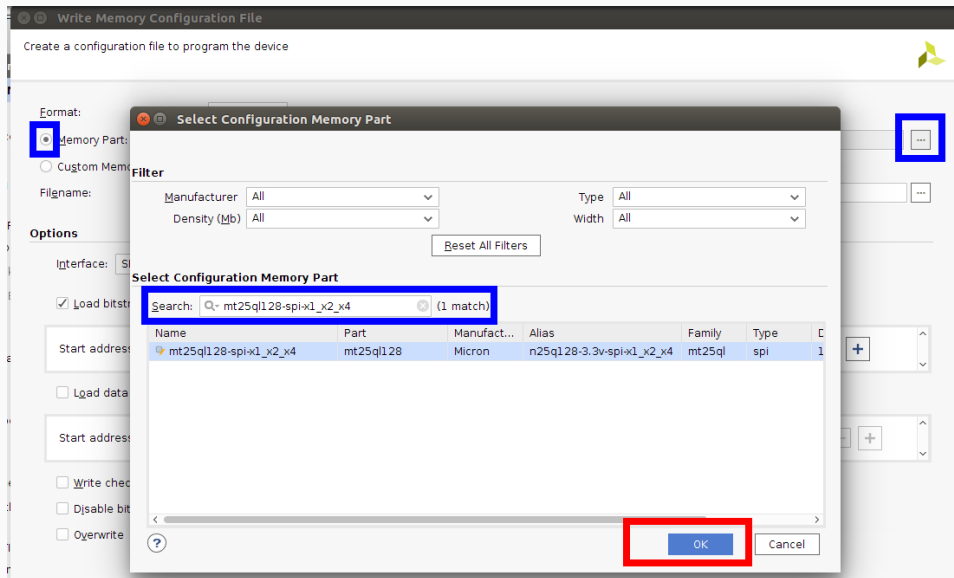

Flash configuration (3) In "Filename" insert the name of file, in

example case **top** and the path of the file. Suggestion: you create the file in the same folder of the bitstream file (.bit).

Memory Part: mt25ql128-spi-x1_x2_x4 ...

Custom Memory Size (MB): 16

Filename: /home/stefano/Documents/Corso VHDL/Laboratori/Lab3/Progetto/counter/counter.runs/impl_1/cnt ...

Options

Interface: SPIx1 v

☒ Load bitstream files ☐ Daisy chain configuration file

Start address: 00000000 Direction: up v Bitfile: o VHDL/Laboratori/Lab3/Progetto/counter/counter.runs/impl_1/cnt.bit ... +

[ide]

Then leave "Interface field" at SPIx1, check "Load bitstream files" and select the bitstream file to be *translated* in .mcs format.



Flash configuration (4) Check "Disable bit swapping" and then "OK".

Format: MCS

☒ Memory Part: mt25ql128-spi-x1_x2_x4

☐ Custom Memory Size (MB): 16

Filename: /home/stefano/Documents/Corso VHDL/Laboratori/Lab3/Progetto/counter/counter.runs/impl_1/top

Options

Interface: SPIx1

☒ Load bitstream files ☐ Daisy chain configuration file

Start address: 00000000 Direction: up Bitfile: /VHDL/Laboratori/Lab3/Progetto/counter/counter.runs/impl_1/top.bit

☐ Load data files

Start address: 00000000 Direction: up Datafile:

☐ Write checksum

☒ Disable bit swapping

☐ Overwrite

Command: `inter/counter.runs/impl_1/cnt.bit } -disablebitswap -file "/home/stefano/Documents/Corso VHDL/Laboratori/Lab3/Progetto/counter/counter.runs/impl_1/top"`















OK

Cancel

Flash configuration (5)

1. Connect the evaluation board to PC by the usb cable.
2. Open Hardware Manager →.
3. Open Target →.
4. Auto Connect.
5. Right Click on "xc7a35t_0 (1)".

 There are no debug cores. [Program device](#) [Refresh device](#)

Hardware	
       	
Name	Status
▼  localhost (1)	Connected
▼  xilinx_tcf/Digilent/210319A...	Open
▼  xc7a35t_0 (1)	Not programmed
 XADC (System Monitor)	

Flash configuration (6)

1. "Add Configuration Memory Device".
2. search "mt25ql128-spi-x1_x2_x4" →.
3. "OK" →.

Add Configuration Memory Device

i Choose a configuration memory part. This can be changed later.

Device: xc7a35t_0

Filter

Manufacturer	All	Type	All
Density (Mb)	All	Width	All

[Reset All Filters](#)

Select Configuration Memory Part

Search: (1 match)


Name	Part	Manufact...	Alias	Family	Type	C
mt25ql128-spi-x1_x2_x4	mt25ql128	Micron	n25ql128-3.3v-spi-x1_x2_x4	mt25ql	spi	1

[?](#) [OK](#) [Cancel](#)



Flash configuration (7)

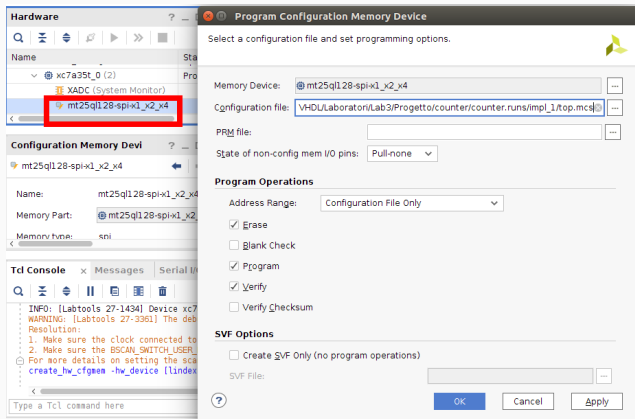1. Right click on the memory device.
2. Program Configuration Memory Device ... →
3. Select the mcs file just created.
4. OK.



Flash configuration (8)

Close the Hardware Manager.

Disconnect the board.

Reconnect it.

Wait ...





Suggested exercises

- Redo 1,2,3, ..., N times the exercises regarding the blink of the led and the slower counter.
- Modify the slower counter exercise in this way :
 1. if SW0 = '0' the counter increments itself else it decrements itself;
 2. if SW1 = '1' the counter doubles its blinking frequency;
 3. if SW2 = '1' the counter halves its blinking frequency;
 4. if SW3 = '1' the counter freezes its state.

