

# Management and analysis of physics datasets, Part. 1

Seventh Laboratory

Stefano Pavinato

20/12/2018

1 Laboratory Introduction

2 Exercise description

3 Homework

1 Laboratory Introduction

2 Exercise description

3 Homework

- Practice with VHDL Moore FSMs.

# VHDL naming convention

Signals/components	Name
Clock	<i>clk</i>
Reset	<i>rst</i>
Input Port	<i>port_in</i>
Output Port	<i>port_out</i>
VHDL file name	<i>entityname.vhd</i>
Test bench file name	<i>tb_entityname.vhd</i>
Signal between 2 comps	<i>sign_cmp1_cmp2</i>
Process name	<i>p_name</i>
state name	<i>s_name</i>
...	...


1 Laboratory Introduction

2 Exercise description

3 Homework

- You have three design source files (*.vhd*) and one constraint file (*.xdc*).
- There is a top module (*top.vhd*), a two pulses generator (*pulses\_generator.vhd*) and a third file (*break\_measure.vhd*).
- You have to write code only in the *break\_measure.vhd* file.

 The VIO core was used in order to generate a reset (*rst*) signal and an *en\_gen* signal. The last signal enables the generation of two pulses. You can substitute the two signals with two switches and/or buttons or you have to generate the VIO core.





```
begin

rst <= vio_rst;
en_trig_in <= vio_en_trig;

gen: pulses_generator
  generic map(PULSE_DIST => 21)
  port map(clk => clk, rst => rst, en_gen_in => en_trig_in, y_out => gen_out);

count : break_measure
  generic map (DONE_TIME => 100000000) -- in number of clock cycles -> 1 second
  port map(clk => clk, rst => rst, pulses_in => pulses_in, count_out => counter, done_out => done_out);


vio1 : vio_1
  PORT MAP (
    clk => clk,
    probe_out0(0) => vio_rst,
    probe_out1(0) => vio_en_trig
  );

end Behavioral;
```

# Two pulses generator (1)


- It was implemented as a Moore FSMs.
- It has three inputs: the clock, the reset and the enable generator *en\_gen* signals. When the reset is done  $0 \rightarrow 1 \rightarrow 0$  and there is a rising edge of the *en\_gen* signal this core generates two pulses.
- This component is configurable with three parameters (*generics*):
  - 1 WTIME: after a time  $WTIME * T_{clock}$  the first pulse is generated;
  - 2 PULSE\_WIDTH: the duration of each pulse is  $PULSE\_WIDTH * T_{clock}$
  - 3 PULSE\_DIST: the second pulse is generated after  $PULSE\_DIST * T_{clock}$  from the falling edge of the first pulse.

# Two pulses generator (2)

 
 
## Circuit description - Board

The pulses at the output of the generator component are the input of the *break\_measure* component. So, if you do not modify the constraint file, you have to short *IO41* with *IO40*.



- You have to write the architecture of the file *break\_measure.vhd*.
- This component has to count the number of clock cycles between the falling edge of the first pulse and the rising edge of the second pulse.
- It has two outputs:
  - 1 *count\_out* : it is an unsigned type. It represents the numbers of clock cycles between the two pulses (It is equals to *PULSE\_DIST*). In order to visualize this value an ILA core has to be instantiated.
  - 2 *done\_out* : it is connected to a led. When the count is done the led has to be on for one second.

- You have to implement a Moore FSM.
- Four states are enough.
- A reverse engineering of the FSM used to implement the two pulses generator can be a source of inspiration.
- The ILA core can be instantiated or in the top module or in the *break\_measure.vhd* file.
- In order to monitor the state of the FSM through the ILA core you can use this example code (copied from the *pulses\_generator.vhd* file):

```
ila : ila_0
  PORT MAP (
    ..
    probe3(0) => y,
    probe3    => std_logic_vector(to_unsigned(state'pos(state_fsm),3))
  );
```

1 Laboratory Introduction

2 Exercise description

3 Homework

- **This homework will be graded.**
- Write a report where there is:
  - 1 the code of the *break\_measure.vhd* architecture;
  - 2 the screenshot of the ILA triggered in the rising edge of the *done\_out* signal;
  - 3 NOTHING ELSE.
- **This homework is for the 15th January.**