Management and analysis of physics datasets, Part. 1

Fifth Laboratory

Stefano Pavinato 6/12/2018



Outline



- 1 Laboratory Introduction
- 2 Arithmetic operations
- 3 Finite Impulse Response filter
- 4 Homework

Outline



- 1 Laboratory Introduction
- 2 Arithmetic operations
- 3 Finite Impulse Response filter
- 4 Homework

Goals



- Some arithmetic operations in VHDL.
- FIR (Finite Impulse Response) filter in VHDL.

VHDL naming convention



Signals/components	Name
Clock	clk
Reset	rst
Input Port	port_in
Output Port	port_out
VHDL file name	entityname.vhd
Test bench file name	tb_entityname.vhd
Signal between 2 comps	sign_cmp1_cmp2
ila signal	ila_signal
vio signal	vio_signal

Outline



- 1 Laboratory Introduction
- 2 Arithmetic operations
- 3 Finite Impulse Response filter
- 4 Homework

Arithmetic operations in VHDL (1)



Or rather, just the arithmetic operations preparatory for this laboratory.

- Numbers are represented as arrays.
- The numbers, in this laboratory, must be signed.
- The arithmetic operations exploited are sum and multiplication.
- The function to convert a *std_logic_vector* signal to a *signed* signal and vice versa are compulsory.
- Uncomment the following library declaration if using
 arithmetic functions with Signed or Unsigned values
 use IEEE.NUMERIC STD.ALL;

Arithmetic operations in VHDL(2)



Declaration

```
signal x : std_logic_vector(N-1 downto 0);
signal s : signed(N-1 downto 0);
```

Conversion

```
x <= std_logic_vector(s);
s <= signed(x);</pre>
```

Arithmetic operations in VHDL (3)



std_logic_vector Assignment

```
x <= "01010110";
x <= x"a6";
```

signed Assignment

```
s <= to_signed(10, N);
s <= to_signed(-10,N);
```

Arithmetic operations in VHDL(3)



- $13 \times 3 = 39$;
- \blacksquare 1101₂ × 11₂ = 100111₂;
- $(4 \text{ elements}) \times (2 \text{ elements}) = 6 \text{ elements};$
- $\blacksquare \Rightarrow$
- (N1 1 downto 0) × (N2 -1 downto 0) = (N1 + N2 1 downto 0);

Arithmetic operations in VHDL (4)



If a number is less than zero:

- $20 \times 0.75 = 15$;
- $\bullet 10100_2 \times 0.11_2 = 1111_2;$
- How realize this operation in VHDL?
- Scale-up the number less than zero of certain quantity Q. For example Q=3.
- $0.11_2 << Q = 110_2$. That is $0.75 * 2^3 = 6$.
- Then: $10100_2 \times 110_2 = 1111000_2$
- Finally scale-down of the same quantity Q, that is $1111000_2 >> Q = 1111_2$. That is $120:2^3 = 15$.

Arithmetic operations in VHDL (5)



If a number is less than zero:

- $20 \times 0.057 = 1.11;$
- But 0.057×2^Q for each Q chosen is never integer. Therefore it is necessary a trade-off between the number of bits and the approximation wished.

Arithmetic operations in VHDL (6)



- In order to do this kind of arithmetic operations is necessary change the dimension of the arrays and scale (up or down) the numbers.
- The numbers in this laboratory are represented as **signed** type.
- You can find a complete list of the operation at this <u>link</u>. Except the sum (+) and the multiplication (*), may be useful two functions:
 - 1 RESIZE:
 - 2 SHIFT_RIGHT.

Outline



- 1 Laboratory Introduction
- 2 Arithmetic operations
- 3 Finite Impulse Response filter
- 4 Homework


FIR filter(1)



Digital Sampled-data Filter implementation



- addition
- multiplication
- delav

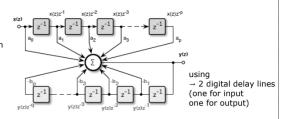

$$\frac{y(z)}{x(z)} = H(z) = \frac{a_0 + a_1 z^{-1} + a_2 z^{-2} + \dots + a_p z^{-p}}{1 + b_1 z^{-1} + b_2 z^{-2} + \dots + b_q z^{-q}},$$

$$y(z) = -(b_1 z^{-1} + b_2 z^{-2} + \dots + b_q z^{-q})y(z) + \dots + (a_0 + a_1 z^{-1} + \dots + a_p z^{-p})x(z).$$

Warning

several sum over variables limited to n-bit values - approximation!

FIR filter(2)



Finite impulse response

From Wikipedia, the free encyclopedia

In signal processing, a finite impulse response (FIR) filter is a filter whose impulse response (or response to any finite length input) is of finite duration, because it settles to zero in finite time. This is in contrast to infinite impulse response (IIR) filters, which may have internal feedback and may continue to respond indefinitely (usually decaying).

The impulse response (that is, the output in response to a Kronecker delta input) of an Nth-order discrete-time FIR filter lasts exactly N + 1 samples (from first nonzero element through last nonzero element) before it then settles to zero.

FIR filters can be discrete-time or continuous-time, and digital or analog.

Contents [hide] 1 Definition

- 2 Properties
- 2 Properties
- 3 Frequency response 4 Filter design
 - 4.1 Window design method
- 5 Moving average example
- 6 See also
- 6 See also 7 Notes
- 8 Citations

Definition [edit]

For a causal discrete-time FIR filter of order N, each value of the output sequence is a weighted sum of the most recent input values:

$$\begin{split} y[n] &= b_0 x[n] + b_1 x[n-1] + \dots + b_N x[n-N] \\ &= \sum_{i=0}^N b_i \cdot x[n-i], \end{split}$$

where:


- x[n] is the input signal,
- y|n| is the output signal,
- . N is the filter order; an Nth-order filter has (N+1) terms on the right-hand side
- b_i is the value of the impulse response at the i'th instant for 0 ≤ i ≤ N of an Nth-order FIR
 filter. If the filter is a direct form FIR filter then b_i is also a coefficient of the filter.

$$x[n]$$
 $y[b]$ $y[b]$ $y[b]$ $y[b]$ $y[b]$

A direct form discrete-time FIR filter of order δ 3. The top part is an N-stage delay line with N+1 taps. Each unit delay is a z^{-1} operator in 2-transform notation.

FIR filter(3)



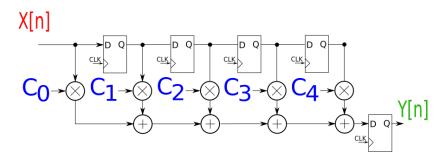

This FIR filter circuit is described by the equation:

$$y[n+1] = \sum_{i=0}^{4} x[n-i] * C_i$$

FIR filter(4)



$$y[n+1] = \sum_{i=0}^{N} x[n-i] * C_i$$

A numerical example. Data:


- $x[n] = 1 \forall n \geq 0 ;$
- $C_0 = 1, C_1 = 2, C_2 = 3, C_3 = 4, C_4 = 5,$

Then:

- y[0] = 0;
- $y[1] = x[0] * C_0 = 1;$
- $y[2] = x[1] * C_0 + x[0] * C_1 = 3;$
- $y[3] = x[2] * C_0 + x[1] * C_1 + x[0] * C_2 = 6$
- $y[4] = x[3] * C_0 + x[2] * C_1 + x[1] * C_2 + x[0] * C_3 = 10$
- $y[5] = x[4] * C_0 + x[3] * C_1 + x[2] * C_2 + x[1] * C_3 + x[0] * C_4 = 15$
- $y[n] = y[5] \forall n \ge 5$

FIR filter type



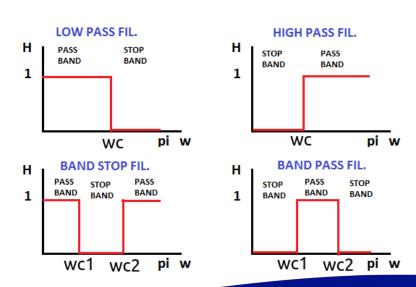

FIR filter coefficients (1)




You can use the python script **coeff.py**. (It is in the folder "utilities"). It exploits the python function firwin.

- It is set to compute the coefficients of a 5 tap digital low-pass filter.
- 5 tap means 5 coefficients.
- 0.1 is the cutt-off frequency, that is $w_c = 0.1 * \pi$. For example a typical sampling frequency of an audio wav file is $f_s = 11025$ Hz. So 0.1 means $f_c = 0.1 * f_s/2 \approx 550$ Hz.
- The script gives the coefficients: $C_0 = C_4 = 0.19335315$, $C_1 = C_3 = 0.20330353$ and $C_2 = 0.20668665$.

FIR filter coefficients (2)



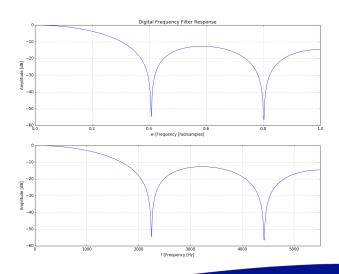

Outline



- 1 Laboratory Introduction
- 2 Arithmetic operations
- 3 Finite Impulse Response filter
- 4 Homework

Homework



- This homework will be graded.
- The frame of the *fir* entity and the frame of the testbench are given. You have to fill them.
- You can implement which type of filter you prefer, with a number of tap greater or equal to 5.
- A behavioral simulation is enough.
- Write a brief report (max. 3 pages), where you describe at least which filter you chose, the value of the coefficients and their conversion in VHDL. Report also a screenshot of the schematic and a screenshot of the testbench simulation result.
- This homework is for the next laboratory.

Hints



- Write the code following the circuit represented in the silde 17.
- 2 Regarding on Flip-Flop remember how to re-use the code with the *component*.
- 3 Do the first testbenches with trivial value of the input and of the coefficients.
- 4 When you have done the point 1, you can set the actual value of the coefficients and re-do the simulation.
- 5 In order to test the correctness of the filter, with the actual coefficients, is better choose values of the input X greater, in absolute value, than 2¹⁰.

Practical example (1)



Not mandatory.

- FIR filter are widely used with audio files.
- In the folder "utilities" there is a .wav file. It's a test file with a frequency sweep from 100 Hz to 3.5 KHz. It was downloaded from youtube and modified. If you want download other wav file, for this laboratory, it is better choose a sampling frequency (f_s) of 11025 Hz.
- In the folder "utilities", there is the script python write_input_txt.py, to convert a mono wav file into a txt file.
- Put the txt file in the vivado project folder ".../proj.sim/sim_1/behav/xsim/".

Practical example (2)



- You need the testbench file *tb_with_file* (it is in the folder "utilities").
- In vivado project settings you have to change the simulation settings, changing the duration of the simulation. 20 ms are enough.



Practical example (3)




- Run the Behavioral simulation.
- Copy the output txt file ("output_file.txt") produced by the testbench in the folder "utilities".
- Run the python script write_filtered_wav.py
- A wav file is created.

Listen the two audio files. Are they different?

Now, if you run the script file **spectrum.py** the frequency spectrum of the audio files are plotted. Meanwhile if you run the file **time_domain.py** the amplitudes of the signals in time domain are plotted.


5-tap LP FIR filter (1)



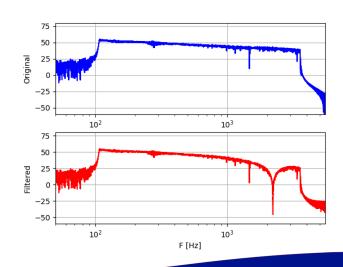


5-tap LP FIR filter (2)



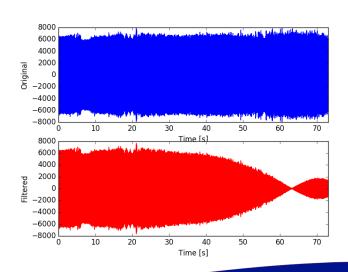

25-tap LP FIR filter (1)



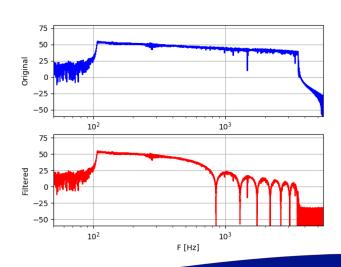

25-tap LP FIR filter (2)



